

# Embedded Dev Transistor Tips

**Shane Trent**

# Conclusion

Low voltage, under 3V - use BJT

Low current, under 500mA - use a BJT (or FET)

High current - use a FET

High speed, above 10kHz - use FET with driver

VERY HIGH POWER, use an IGBT

# Why Use Transistors?

Switch higher current

Switch higher voltage

Invert signal

Translate voltage levels

Buffer outputs (PWM to Linear voltage)

# Transistor as Switches

BJT - good for low power

MOSFET - good for high-current


IGBT\* - best for high-voltage, high-power

# Minimum NPN Switch

Always need base resistor!

$$V_{be} > 0.6V$$

$$I(b) = (5V - 0.6V) / 1k$$

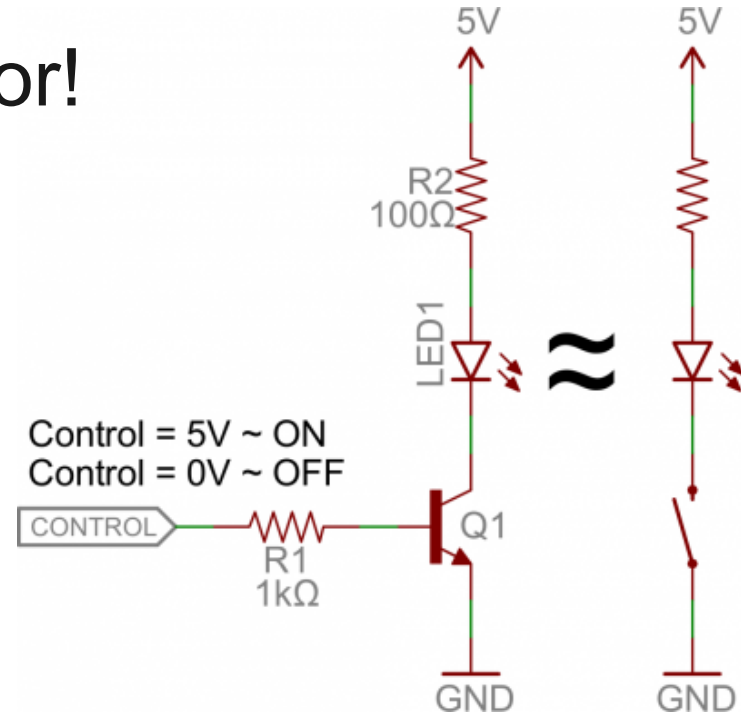


# N-FET Inductive Load

Low  $R_{ds}$

Pull-down (100k) essential


Gate resistor (100) good idea

D3 for inductive kick

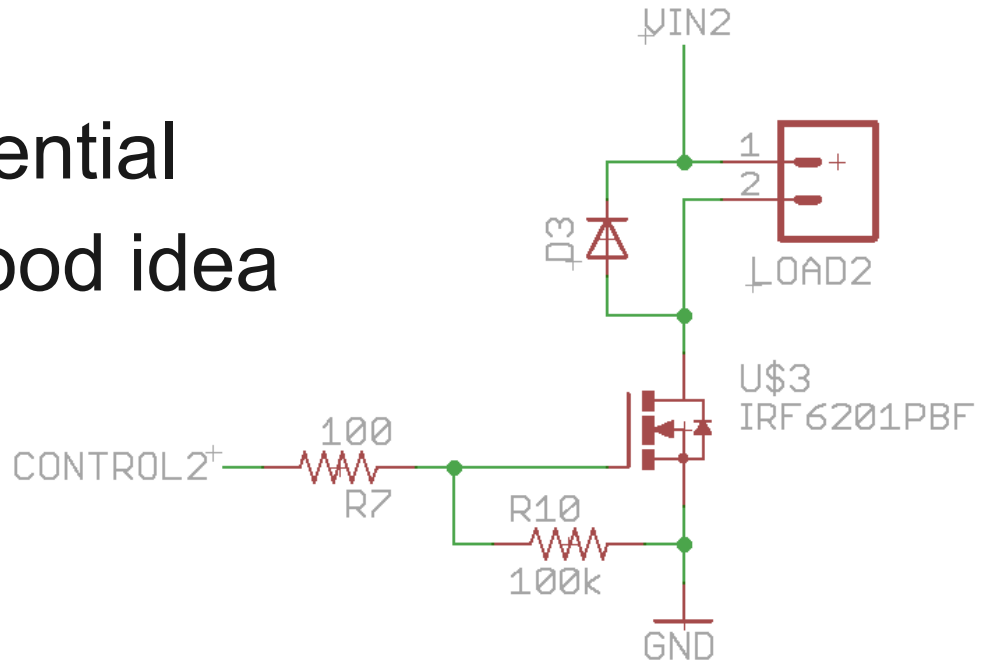

# BJT Inverter - Shifter

Sensitive FET also

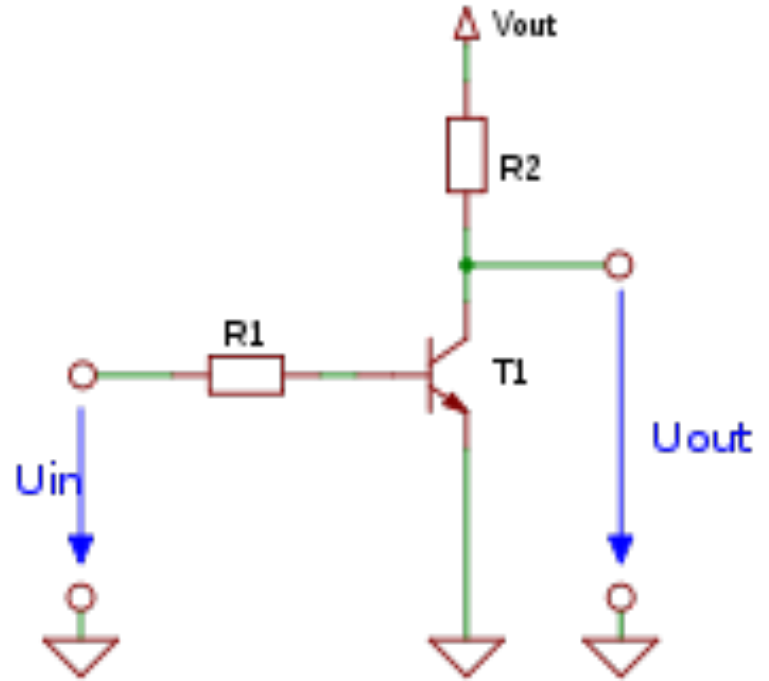

# Clever Level Converter


Bi-directional!

Uses body diode

Requires  $HV-LV > 0.6V$

Philips - AN97055

Sparkfun - Level

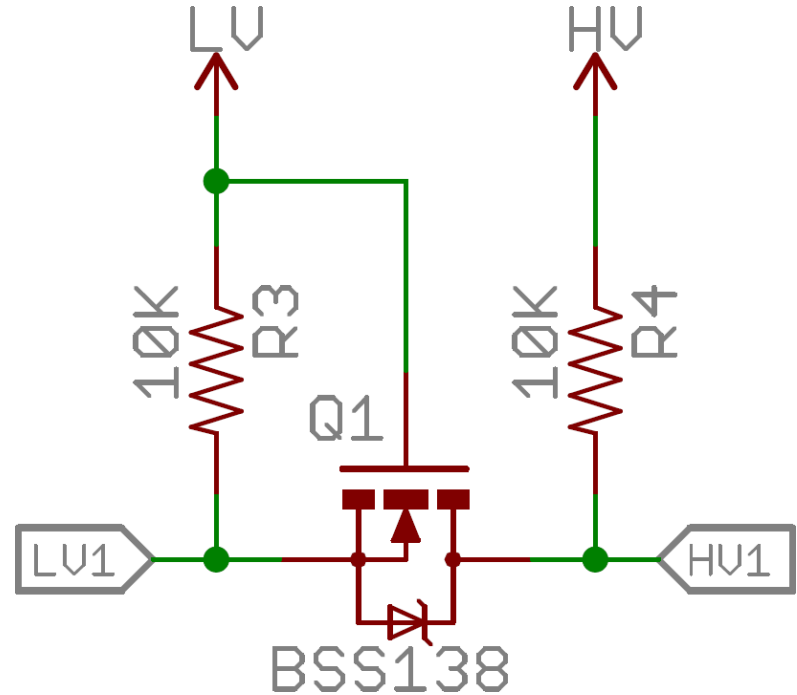




# Buffer (with Low-Pass)



PWM-> Analog

BJT more linear

FET not low  $R_{ds}$

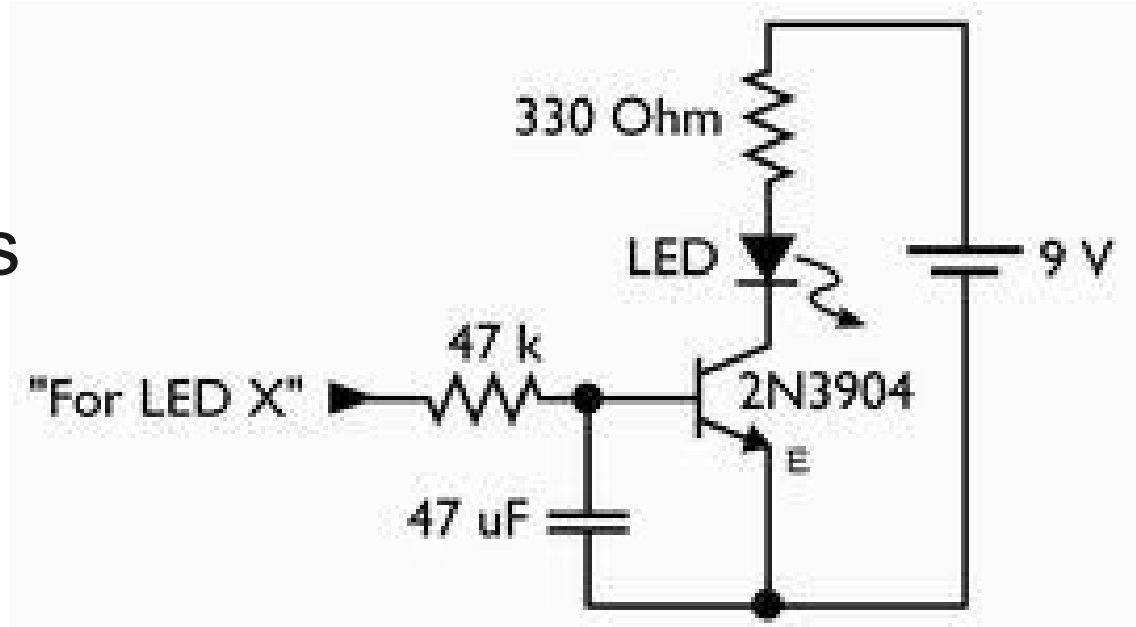

# Level Up - Current Limiter

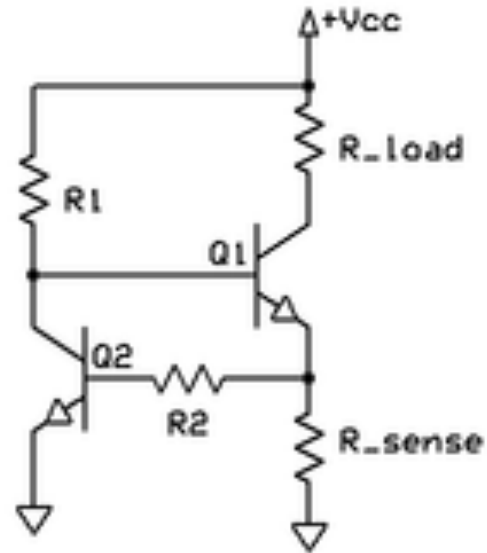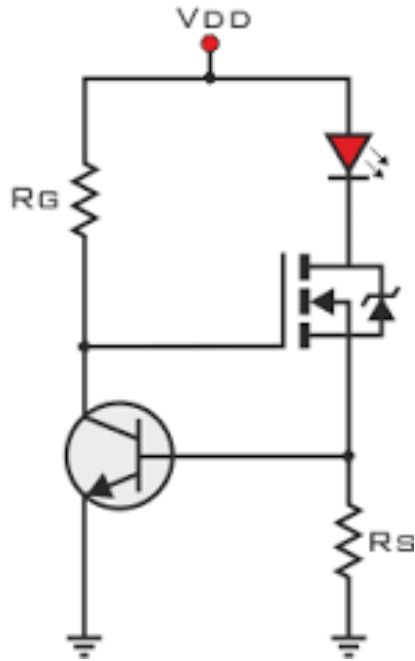

# How to Kill a Transistor

Exceed Voltage/Current Rating

Forget to use base resistor on BJT

Underdrive the gate of a FET

Exceed the device power dissipation limits

# BJT in a Nutshell

Current driven devices

$V_{ce(sat)} < 200\text{mV}$


$V_{be} \sim 0.6\text{V}$

Base current is multiplied

Susceptible to thermal runaway

Darlington  $V_{be} \sim 1.4\text{V}$

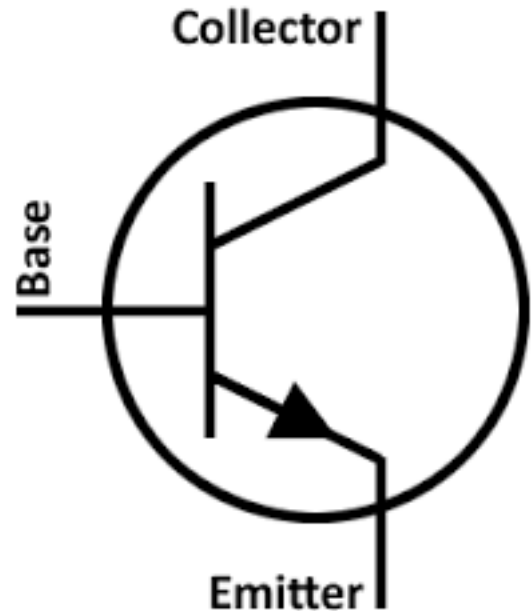Darlington  $V_{ce(sat)} \sim 0.85\text{V}$



# MOSFET in a Nutshell

Voltage driven devices


On resistance can be  $< 1$  mOhm

Requires min gate voltage

Very fast with proper gate drive

High current at low losses

Resists thermal runaway (can parallel)

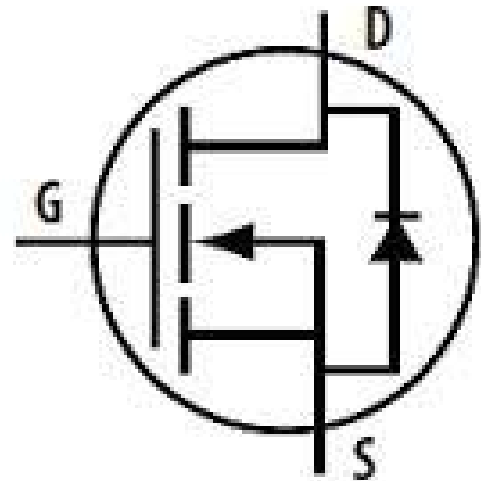



# IGBT in a Nutshell

Love child of BJT and MOSFET



Combines low saturation voltage of BJTs with the voltage drive of MOSFETs

Invented by Dr. Jayant Balaga in 1977  
(currently ECE Professor at NCSU)

# IGBT - Very High Power

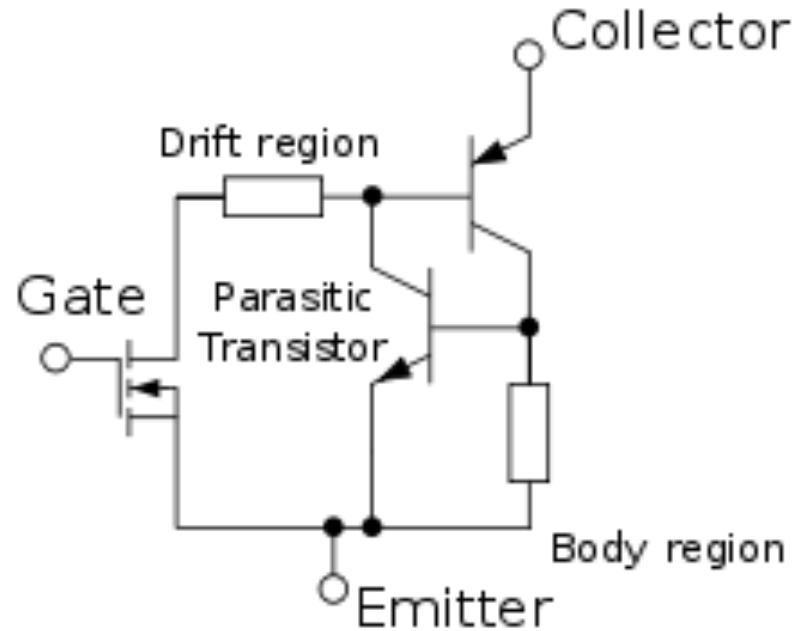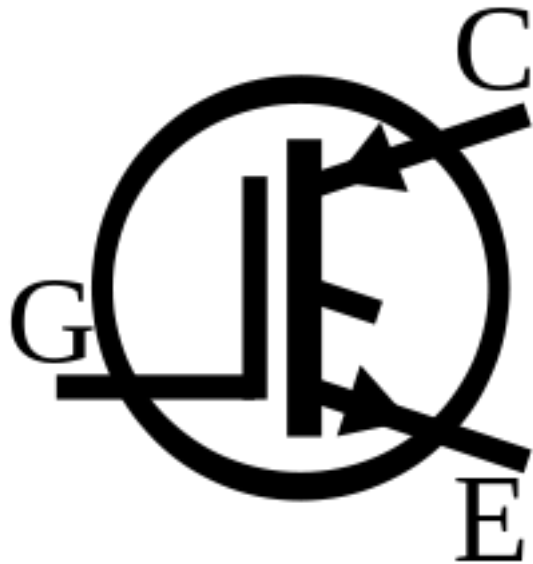

# BJTs - NPN vs PNP

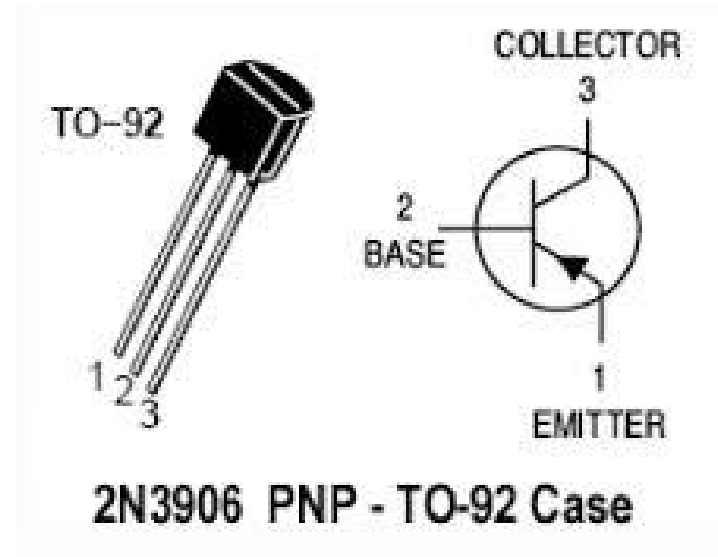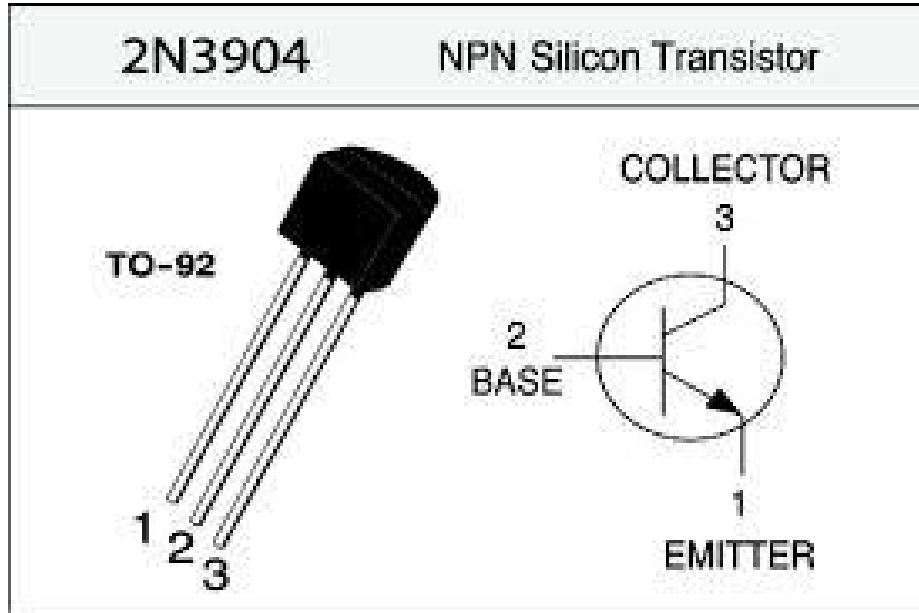



# BJT top Parameters

Voltage (Collector-Emitter)

Collector Current

DC Current gain ( $h_{FE}$ ) (and Darlington)

Less critical:  $V_{BE(sat)}$  and  $V_C(sat)$

Similar for many BJTs (0.6V and 0.1-0.2V)

# BJTs Easy to Substitute

Same or higher Collector-Emitter voltage

Same or higher current rating

Same type (NPN vs PNP vs Darlington)

limitations are special gain or frequency

# MOSFET top Parameters

V<sub>ds</sub> (drain-source)

Current Rating

Resistance (drain-source) (the “ON” resistance)

Gate sensitivity (logic level?)

Numbers vary from vendor to vendor

Must look at the charts!

# MOSFET Substitution

Same or higher  $V_{ds}$  and current rating

Same or lower gate drive (logic level?)

Same type (N-FET vs P-FET)

limitations are gate capacitance and speed

# Questions?

# Resources

The Art of Electronics (any edition, 4th Ed is current)

<https://learn.sparkfun.com/tutorials/transistors>

<https://www.adafruit.com/datasheets/an97055.pdf>

<https://learn.sparkfun.com/tutorials/bi-directional-logic-level-converter-hookup-guide>

<http://www.evilmadscientist.com/2006/make-a-cylon-jack-o-lantern/>

[https://en.wikipedia.org/wiki/Insulated\\_gate\\_bipolar\\_transistor](https://en.wikipedia.org/wiki/Insulated_gate_bipolar_transistor)

<http://www.ece.ncsu.edu/people/bjbaliga>